

**Computer Organization & Architecture Laboratory**

**Subject Code: PCC-CS492**

**ASSIGNMENT – I**

**Submission Date: 09.03.2022**

1. Write the VHDL programs to implement all the basic gates: i) OR, ii) AND, iii) NOT.
2. Write the VHDL programs to implement universal gates: i) NAND, ii) NOR.
3. Write the VHDL programs to implement i) XOR, ii) XNOR.
4. Design i) Half adder and ii) Full adder using VHDL.
5. Design i) Half subtractor and ii) Full subtractor using VHDL.

**Note: Write the program in A4 page and draw the simulation result for every individual program. Submit the assignment in channel file.**